

Part 2: MAE 10 6 Midterm 2009

1. An oscilloscope is used to measure this:

- a) voltage b) resistance c) current d) capacitance

2. An op amp is always described by which set of equations (choose the most complete set, and assume $K > 0$),?

- a) $V_+ = V_-$; $i_+ = i_- = 0$; $V = K(V_+ - V_-)$
 b) $V_+ = V_-$; $i_+ = i_- = 0$; $V = -K(V_+ - V_-)$
 c) $V = K(V_+ - V_-)$
 d) $i_+ = i_- = 0$; $V = K(V_+ - V_-)$
 e) $i_+ = i_- = 0$

$V_+ = V_-$ only if connected with negative feedback

3. What is the period of a sine wave with a frequency equal to π Hz?

- a) 2π sec b) $1/(2\pi\pi)$ sec c) $2\pi\pi$ sec d) $1/\pi$ sec

4. A band-pass filter attenuates:

- a) high frequencies b) a band of frequencies c) low frequencies d) high and low frequencies

5. A first-order, low-pass filter causes a phase lag in a sinusoidal input. The amount of phase lag at a frequency much greater than the cut-off frequency is:

- a) 90 deg b) 180 deg c) 45 degrees d) 70.7 deg e) 0 deg

6. The time constant of a first-order system tells when the output has gotten how far along the way to its final value?

- a) 37% b) 10% c) 63% d) 90% e) 33%

7. If you put a sine wave into a linear system, the output could be (choose the most complete answer):

- a) bigger, smaller, or a constant, phase shifted, at a different frequency
 b) smaller, phase shifted, and at the same frequency
 c) bigger, smaller, and at a different frequency
 d) bigger, smaller, or a constant, phase shifted, at the same frequency
 e) bigger or smaller and at the same frequency


Note: If gain = 0 output will be a constant

For the next 7 problems, choose from these letters:

- a. Feedback controller advantage
 b. Feedback controller disadvantage
 c. Feedforward controller advantage
 d. Feedforward controller disadvantage

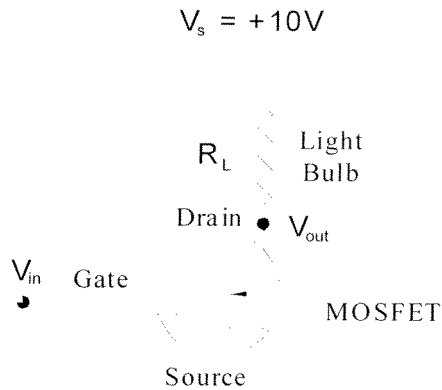8. Requires an accurate model of the plant **D**
 9. It has to allow an error to develop before it does anything **B**
 10. Delay causes it to go unstable **B**
 11. It only requires basic knowledge of the plant **A**
 12. It can theoretically produce error-less control **C**
 13. It requires a sensor **B**
 14. It can cancel unexpected disturbances **A**

A circuit for controlling a light bulb with a MOSFET is shown below. The light bulb is modeled as a resistor. By changing the input gate voltage to the MOSFET, the light bulb can be turned on and off. A table of the MOSFET's drain/source resistance (like the one you generated in lab) is also shown.



V_{in} (volts)	R_{DS} (ohms)
0	100
1	100
2	90
3	80
3.4	75
3.6	41
3.9	4
4.2	0.1
5	0.01

15. Assume the light-bulb shines the brightest when the most current goes through it. It will shine the brightest when the input gate voltage (V_{in}) is:

- a) 0 volts **b) 5 volts** c) 3.4 volts d) 1 volt e) 4.2 volts

16. Assume $R_L = 3996$ ohms. Calculate V_{out} corresponding to an input gate voltage of 3.9 volts.

First significant digit of V_{out} :

- a) 0 **b) 1** c) 2 d) 3 e) 4

times 10 to the what power?

- a) 1 b) 0 c) -1 **d) -2** e) doesn't matter

$$V_o = \left(\frac{4}{4 + 3996} \right) 10$$

$$= \frac{1}{1000} 10 = .01 \text{ V}$$

$$= 1e^{-2} \text{ V}$$

17. Approximately how much current enters the gate?

First significant digit of V_{out} :


- a) **0** b) 1 c) 2 d) 3 e) 4

times 10 to the what power?

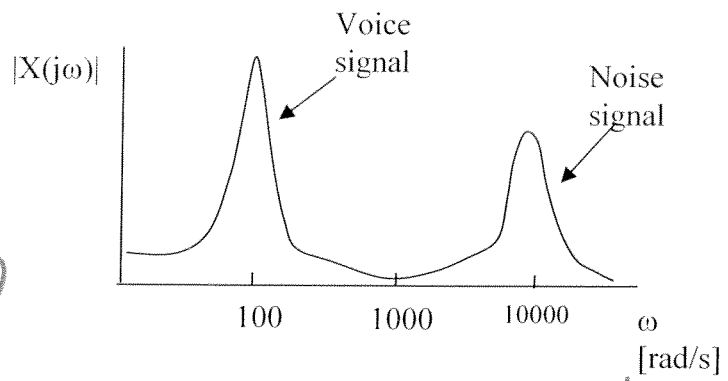- a) 1 b) 0 c) -1 d) -2 **e) doesn't matter**

Shown below is the frequency spectrum of a noisy speech signal. Design a RC low pass filter using your tool-box contents to get rid of the noise.

Toolbox Contents:
 $R = 1\Omega, 10\Omega, 100\Omega, 1\text{ K}\Omega$
 $C = 1\text{ pF}, 0.1\ \mu\text{F}, 1\ \mu\text{F}$



18. Value for R

- a) 1Ω b) 10Ω c) 100Ω **d) $1\text{ K}\Omega$**


19. Value for C

- a) $1.0\ \mu\text{F}$** b) $0.1\ \mu\text{F}$ c) $0.01\ \mu\text{F}$ d) $0.001\ \mu\text{F}$

desire $\omega_c = 1000 = \frac{1}{RC}$

$$RC = .001 = 1\text{ K}\Omega \times 1e^{-6} \text{ F}$$

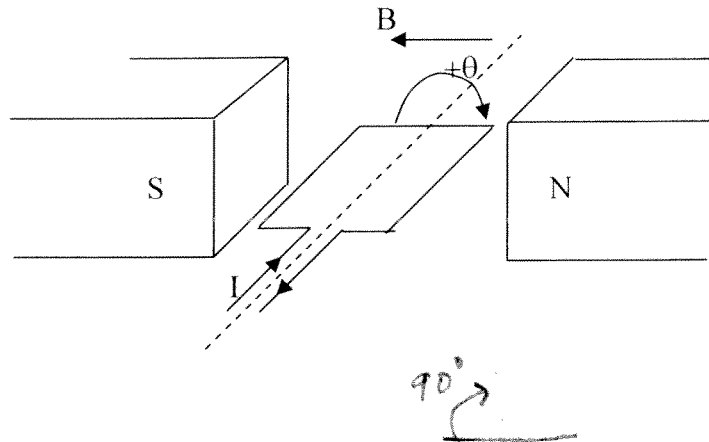Shown below is a diagram of a DC brushed motor. Assume that the commutation stops working, such that current flows only in the direction shown.



20. At what angle θ will the armature come to rest? Assume the armature is initially at $\theta = 0^\circ$ as shown when the commutation fails, and that positive θ is defined clockwise looking into the page, as shown.

- a) 0 degrees
- b) 180 degrees
- c) 270 degrees
- d) -90 degrees
- e) 90 degrees


21. Which of the following is part of the commutation mechanism?

- a) shaft
- b) armature
- c) brushes
- d) magnet
- e) coils

22. Assume the motor is working and the motor's torque constant and back EMF constant is B , internal resistance is R , and inductance L . Assume you hold the shaft fixed, and apply a voltage V . What is the final torque you will feel?

- a) V/B
- b) BV/R
- c) L/R
- d) V/R
- e) VR/B

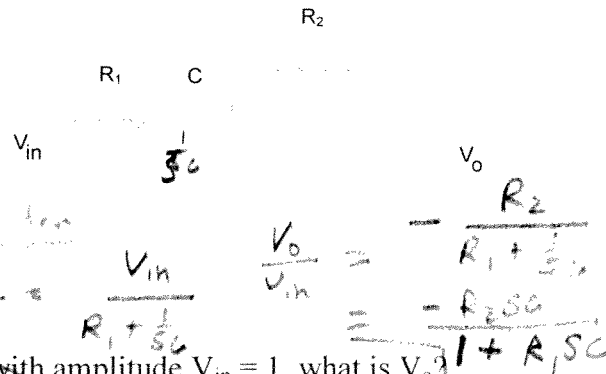23. For the circuit shown to the right, assume $R_1 = R_2 = 1 \text{ Kohm}$, and $C = 0.5 \mu\text{F}$. For a constant input $V_{in} = 1 \text{ V}$, what is the magnitude of V_o ?



First significant digit of V_o :

- a) 0
 - b) 1
 - c) 2
 - d) 3
 - e) 4
- times 10 to the what power?
- a) 1
 - b) 0
 - c) -1
 - d) -2
 - e) doesn't matter

ind transfer fun

$$\frac{-V_o}{R_2} = \frac{V_{in}}{R_1 + \frac{1}{sC}}$$

$$\frac{V_o}{V_{in}} = -\frac{R_2}{R_1 + \frac{1}{sC}}$$

$$= -\frac{R_2 sC}{1 + R_1 sC}$$

24. For the same circuit, for a very high frequency sinusoid with amplitude $V_{in} = 1$, what is V_o ?

- a) 0
- b) -1
- c) 1
- d) 2
- e) -2

let $s \rightarrow \infty$ (constant part)


$$\frac{V_o}{V_{in}} = \frac{0}{1}$$

25. times 10 to the what power?

- a) 1
- b) 0
- c) -1
- d) -2
- e) doesn't matter

26. What is this circuit?

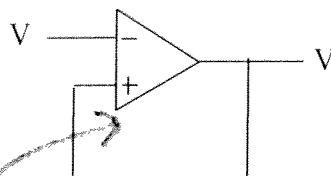- a) adder
- b) useless
- c) buffer
- d) subtractor
- e) amplifier




positive feedback

let $s \rightarrow \infty$

$$\frac{V_o}{V_{in}} = -\frac{R_2 C}{R_1 C} = -1$$


23
33

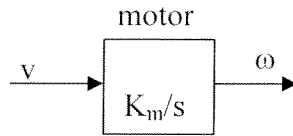You want to control the speed of a motor. You are using a current amplifier with the motor, so the speed is related to the input voltage to the current amplifier by the following transfer function:



where v is the voltage input to the motor and ω is the angular velocity of the shaft and K_m is a constant.

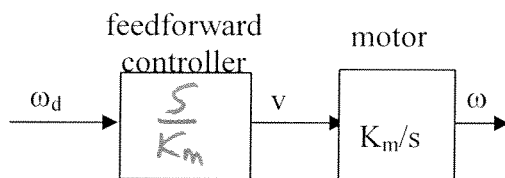Shown below is a block diagram of an open-loop (i.e. feedforward) controller for the motor, where ω_d is the desired output of the motor. What transfer function should the controller box have to make the output equal the desired output?




27. Numerator of transfer function

- a) s b) v c) ω_d d) ω e) K_m

28. Denominator of transfer function

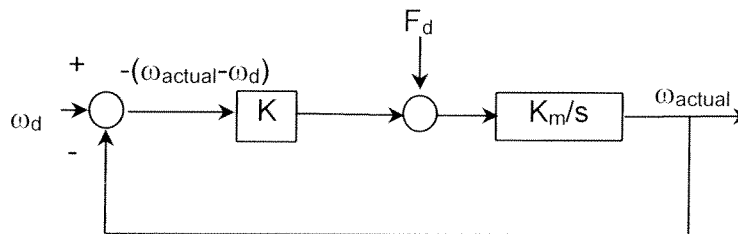- a) s b) v c) ω_d d) ω e) K_m

One of the major benefits of feedback is its ability to cancel the effects of unmodeled “disturbances”. Assume you build a feedback controller, but there is a disturbance force F_d affecting the motor:



You can view the effect of F_d on ω_{actual} as being described by a sort of filter.

29. What type of filter is it?

- A. Band pass B. High pass C. Notch D. Motor e) Low pass

30. What values do you have to make big to eliminate the effect of the disturbance?

- a) s b) K c) K_m d) K or K_m e) s or K

to see this: find transfer fn.

$$\omega_a = \frac{K_m}{s} (F_d + K(\omega_d - \omega_a))$$

$$\omega_a (1 + \frac{K_m K}{s}) = \frac{K K_m}{s} \omega_d + \frac{K_m}{s} F_d$$

$$\omega_a = \frac{K K_m}{s + K_m K} \omega_d + \frac{K_m}{s + K_m K} F_d$$

make big to cancel F_d